

e. Inc. All rights reserved

(CRD15DD17P)

Wide Input Voltage Range (300VDC-1200VDC) 15W Flyback Auxiliary Power Supply Board

(0:0)



OVERVIEW OF CREE'S CRD15DD17P 15 W AUXILIARY POWER SUPPLY BOARD

- CRD15DD17P, 15 W flyback auxiliary power supply board is based on Cree's 1700 V, 1000 mΩ SiC MOSFET with high blocking voltage capability
- Due to low blocking voltage capability of Si MOSFET, it is very challenging to use them in these kind of applications
- The main target applications of this reference design board are solar power, energy storage and traction industry
- Cree's 1700 V, 1000 mΩ SiC MOSFET in a TO-263-7 package has been utilized due to the availability of it's high creepage (~ 7 mm) distance







DESIGN SPECIFICATIONS

• The design specifications of CRD15DD17P, 15 W flyback auxiliary power supply board are mentioned in the following table:

| Parameters | Values | |
|-----------------------------------|---|--|
| Input voltage range, 50-60Hz | 480 VAC - 530 VAC or 300 VDC - 1200 VDC | |
| Output voltage | 12 VDC | |
| Output Current | 1.3 A | |
| Output Power | 15 W | |
| Switching frequency | 100 kHz (max) | |
| Efficiency | > 85% | |
| Max ambient operating temperature | 50 ° C | |
| Topology | Single-end Flyback | |
| Power devices package | TO-263-7 | |



PHYSICAL DIMENSIONS AND THE PINOUTS OF CREE'S CRD15DD17P 15 W AUXILIARY POWER SUPPLY BOARD

• The physical dimensions and the pinouts of CRD15DD17P, 15 W flyback auxiliary power supply board are:

64 mm (L) X 45 mm (W) X 25 mm (H)











ELECTRICAL OPERATION


- CRD15DD17P, 15 W auxiliary power supply board consists of a traditional single switch flyback topology.
- Both AC or DC power source with a voltage range of 480 VAC 530 VAC / 300 VDC 1200 VDC can be applied directly to the input of CRD15DD17P, 15 W auxiliary power supply board.
- Primary side of the flyback transformer consists of Cree's 1700 V, 1000 mΩ SiC MOSFET, Texas Instruments UCC28740 flyback controller IC and the feedback circuit.
- Secondary side of the flyback transformer uses 150 V/3A Schottky diode with a closed loop voltage feedback.

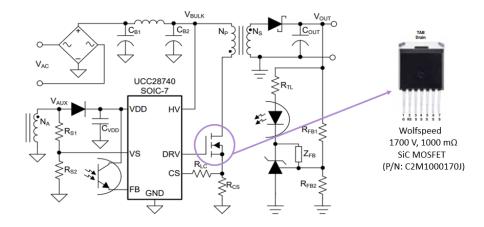

ELECTRICAL OPERATION (Continued)

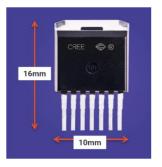- Cree's 1700 V, 1000 mΩ SiC MOSFET has been utilized in CRD15DD17P, 15 W auxiliary power supply board
- Main features are listed below:
 - High Blocking Voltage
 - High Creepage Distance (~ 7 mm)
 - Low Source Inductance due to Kelvin Source availability
 - Low RDS(on) Change over Temperature
 - High Frequency Operation



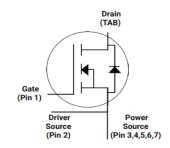




ELECTRICAL OPERATION (Continued)

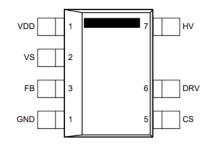- Texas Instruments UCC28740 Flyback controller IC has been utilized in CRD15DD17P, 15 W auxiliary power supply board
- Main features are listed below:
 - No Load Power Consumption < 10 mW</p>
 - Opto-Coupled Feedback
 - ➤ ± 1% of Voltage Regulation across Line and Load
 - Valley Switching Operation to Reduce Switching Loss
 - Overvoltage and Overcurrent Protection Functions









PERFORMANCE DATA (EFFICIENCY)

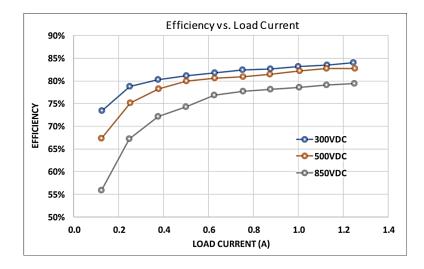- Cree' CRD15DD17P, 15 W auxiliary power supply board is tested up to full load under the input voltage levels of 300VDC, 500 VDC, 850 VDC, 1100 VDC and 1200 VDC.
- The maximum efficiency achieved by Cree's CRD15DD17P, 15 W auxiliary power supply board is 85 % at 300 VDC.




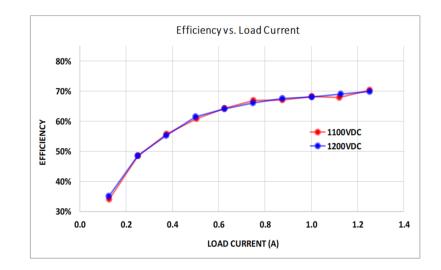




PERFORMANCE DATA (VOLTAGE REGULATION)

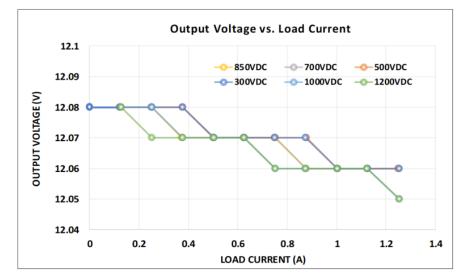- Cree's CRD15DD17P, 15 W auxiliary power supply board is tested under various load conditions and at various input voltage levels.
- Under all those conditions, the overall voltage regulation of Cree's CRD15DD17P, 15 W auxiliary power supply board is within 0.25 %



PERFORMANCE DATA (EMI)

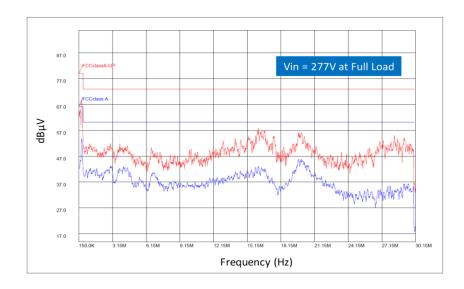
- Conducted EMI of Cree's CRD15DD17P, 15 W auxiliary power supply board has been measured at full load while the input voltage fixed at 277 VAC
- Under these conditions, Cree's CRD15DD17P, 15 W auxiliary power supply board passed FCC Part 15 Class A standard for commercial applications






PERFORMANCE DATA (15 W Load @ 300 VDC Input)

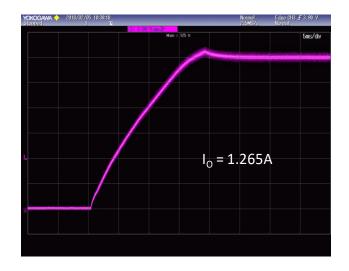
- Performance of Cree's CRD15DD17P, 15 W auxiliary power supply board can be evaluated by the output voltage waveforms both at full load and no load conditions
- Following are the spike-less output voltage waveforms that have been captured at 300 VDC input both under full load and no load conditions.




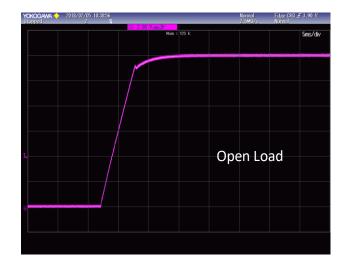

PERFORMANCE DATA (15 W Load @ 1200 VDC Input)

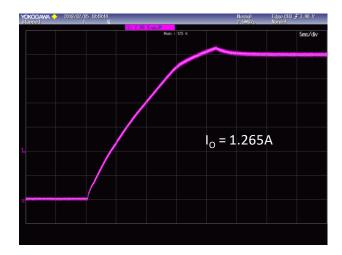
- Performance of Cree's CRD15DD17P, 15 W auxiliary power supply board can be evaluated by the output voltage waveforms both at full load and no load conditions
- Following are the spike-less output voltage waveforms that have been captured at 1200 VDC input both under full load and no load conditions.



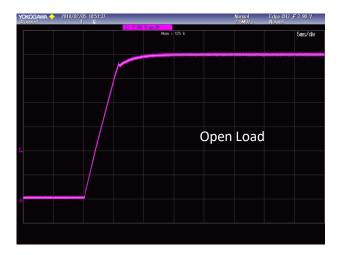

PERFORMANCE DATA (Thermal Measurements)

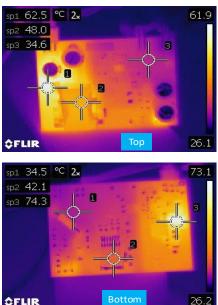 Performance of Cree's CRD15DD17P, 15 W auxiliary power supply board can be evaluated by the thermal measurements as well. Following thermal images show that under each condition, all components on the board operate well below their thermal limits




(Full Load @ 300 VDC Input)

♦ FLIR Wolfspeed. A CREE COMPANY Downloaded from Arrow.com.



(Full Load @ 1200 VDC Input)



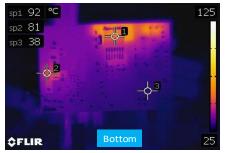

SUMMARY

- CRD15DD17P, 15 W flyback auxiliary power supply board demonstrates efficient operation of Cree's 1700 V, 1000 mΩ SiC MOSFET that has high blocking voltage and high creepage distance (~ 7mm) availability
- Wolfspeed's 15 W flyback auxiliary power supply board can accept a wide range of AC or DC input voltage (480 VAC 530 VAC) or (300 VDC 1200 VDC) and provide 12 VDC at the output with an exceptional efficiency of 85 %
- Simple control approach has been utilized to reduce the overall complexity and cost of the system
- High-frequency operation of Wolfspeed's 1700 V, 1Ω SiC MOSFET has been demonstrated as well that helps in reducing form factor of the board significantly.
- High performance data of CRD15DD17P, 15 W flyback auxiliary power supply board demonstrates the effective utilization of Cree's 1700 V, 1000 mΩ SiC MOSFET for high voltage applications

(If user require more information about the detailed operation of Cree's CRD15DD17P, 15 W auxiliary power supply board please review Cree's CRD15DD17P, 15 W auxiliary power supply board's Application Note)

(If user have questions about Cree's CRD15DD17P, 15 W auxiliary power supply board, please contact Cree at <u>sic_power@cree.com</u>)



CREE COMPANY © 2018 Cree, Inc. All rights reserved

APPENDIX


- Schematic of Cree's CRD15DD17P, 15 W auxiliary power supply board
- Package Contents of Cree's CRD15DD17P, 15 W auxiliary power supply board

(If user require more information about the detailed operation of Cree's CRD15DD17P, 15 W auxiliary power supply board please review Cree's CRD15DD17P, 15 W auxiliary power supply board's Application Note)

(If user have questions about Cree's CRD15DD17P, 15 W auxiliary power supply board, please contact Cree at sic power@cree.com)



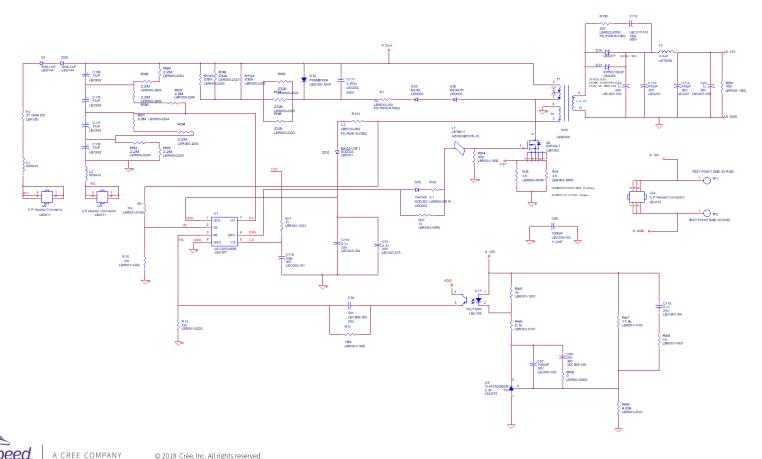SCHEMATIC OF Cree's CRD15DD17P, 15 W AUXILIARY POWER SUPPLY BOARD



© 2018 Cree, Inc. All rights reserved

Wolfspeed Downloaded from Arrow.com

PACKAGE CONTENTS OF Cree's CRD15DD17P, 15 W AUXILIARY POWER SUPPLY BOARD

| Item 💌 | Qty Per 💌 | Reference designate | Description | Manufacturer Name | Manufacturer P/N |
|--------|-----------|--------------------------------------|--|--|---------------------|
| 1 | 2 | C22,C23 | CAP CER 1µF 50V X7R 0805 | Murata Electronics North America | GRM21BR71H105KA12L |
| 2 | 1 | C67 | CAP CER 1000pF 50V 10% 0805 X7R | KEMET | C0805C102K5RACTU |
| 3 | 1 | C73 | CAP CER 4.7µF 25V X7R 0805 | Taiyo Yuden | TMK212AB7475KG-T |
| 4 | 2 | C94,C95 | CAP CER 0.033µF 50V X7R 0603 | AVX CORP. | 06035C333KAT2A |
| 5 | 1 | C96 | CAP FILM 1000pF 20% 1.25kVDC RAD | KEMET | PHE850EA4100MA01R17 |
| 6 | 4 | C115,C117,C109,C110 | CAP ALUM 15µF 20% 450V RADIAL | Rubycon | 450BXW15MEFC10X20 |
| 7 | 1 | C111 | CAP CER 0.033µF 630V X7R 1206 | TDK Corporation | C3216X7R2J333K160AA |
| 8 | 1 | C112 | CAP CER 100pF 500V X7R 1206 | KEMET | C1206C101KCRACTU |
| 9 | 2 | C113,C114 | CAP ALUM 470µF 20% 25V RADIAL | Panasonic Electronic Components | EEU-EB1E471 |
| 10 | 1 | C118 | CAP CER 100PF 16V X7R 0603 | AVX Corporation | 0603YC101KAT2A |
| 11 | 2 | C116. C119 | CAP CER 0.1µF 25V X7R 0603 | Murata Electronics North America | GRM188R71E104KA01D |
| 12 | 1 | D10 | DIODE GEN PURP 250V 200mA SOD323 | ON Semiconductor | BAS21HT1G |
| 13 | 2 | D25.D26 | DIODE GEN PURP 1kV 1A DO214AC | MICRO COMMERCIAL COMPONENT | FS1M-TP |
| 14 | 2 | D1,D28 | DIODE GEN PURP 1KV 1A SMA | Diodes Incorporated | S1M-13-F |
| 15 | 1 | D30.D31 | DIODE SCHOTTKY 150V 3A SMBFLAT | STMicroelectronics | STPS3150UF |
| 16 | 1 | D35 | DIODE GEN PURP 75V 150mA SOD323 | MICRO COMMERCIAL COMPONENT | 1N4148WXTPMSTR |
| | | | Metal Film Resistor Through Hole 2W 27 ohm | | 11111101111111011 |
| 17 | 1 | F2 | 10% FUSIBLE | TT ELECTRONICS | EMC2-27RKI |
| 18 | 2 | J22,J23 | 4 Positions Header Connector, 0.100" (2.54mm), Through Hole, Right Angle, Tin | SAMTEC INC USA | TSW-102-09-T-D-RA |
| 19 | 1 | J24 | 6 Positions Header Connector, 0.100" (2.54mm), Through Hole, Right Angle, Tin | SAMTEC INC USA | TSW-103-09-T-D-RA |
| 20 | 2 | L1,L2 | FIXED IND 8.2mH 100mA 16Ω TH | Wurth Electronics Inc. | 744731822 |
| 21 | 1 | L3 | FIXED IND 3.3μH 4.5A 20 mΩ SMD | Bourns Inc. | SDR0805-3R3ML |
| 22 | 1 | L7 | FERRITE BEAD 750Ω 0603 1LN | Laird-Signal Integrity Products | HZ0603B751R-10 |
| 23 | 1 | Q2 | MOSFET N-CH 1700V 5.3A Surface Mount D2PAK (7-Lead) | Wolfspeed | C2M1000170J |
| 24 | 1 | R1 | RES SMD 10Ω 5% 2/3W 1206 | Panasonic Electronic Components | ERJ-P08J100V |
| 25 | 1 | R7 | RES SMD 51kΩ 1% 1/10W 0603 | Yageo | RC0603FR-0751KL |
| 26 | 1 | R10 | RES SMD 14kΩ 1% 1/10W 0603 | Panasonic Electronic Components | ERJ-3EKF1402V |
| 27 | 3 | R11,R45,R46 | RES SMD 1kΩ 1% 1/4W 0603 | Vishay Dale | CRCW06031K00FKEA |
| 28 | 1 | R13 | RES SMD 196kΩ 1% 1/10W 0603 | Vishay Dale | CRCW0603196KFKEA |
| 29 | 1 | R14 | RES SMD 22kΩ 1% 1/10W 0603 | Panasonic Electronic Components | ERJ-3EKF2202V |
| 30 | 1 | R37 | RES SMD 10Ω 1% 1/8W 0805 | Panasonic Electronic Components | ERJ6ENF10R0V |
| 31 | 2 | R38.R39 | RES SMD 3.9Ω 1% 1/8W 0805 | Vishay Dale | CRCW08053R90FKEA |
| 32 | 1 | R47 | RES SMD 17.4kΩ 1% 1/10W 0603 | Yageo | RC0603FR-0717K4L |
| 33 | 1 | R48 | RES SMD 4.53kΩ 1% 1/10W 0603 | Panasonic Electronic Components | ERJ-3EKF4531V |
| 34 | 1 | R49 | RES SMD 4.33K21% 1/10W 0603 RES SMD 5.1k Ω 1% 1/10W 0603 | Panasonic Electronic Components | ERJ-3EKF5101V |
| 35 | 2 | R50.R54 | RES SMD 3.1K 22 1% 1/10W 0603 RES SMD 10kΩ 1% 1/10W 0603 | Panasonic Electronic Components | ERJ-3EKF1002V |
| 36 | 1 | R56 | RES SMD 10kH 1/kH 1/10W 0005 RES SMD 0Ω JUMPER 1/4W 0603 | Vishay Dale | CRCW06030000Z0EA |
| 37 | 1 | R52 | RES SMD 5.1Ω 1% 1/8W 0805 | Panasonic Electronic Components | ERJ-6RQF5R1V |
| 38 | 8 | R88,R89,R90,R91,R92,R 93,R94, R95 | RES SMD 2.2MΩ 1% 1/4W 1206 | Vishay Dale | CRCW12062M20FKEA |
| 39 | 6 | R96,R97,R98,R99,R102, R103 | RES SMD 232kΩ 1% 1/4W 1206 | Panasonic Electronic Components | ERJ-8ENF2323V |
| 40 | 1 | R100 | RES SMD 200Ω 1% 3/4W 2010 | Vishay Dale | CRCW2010200RFKEF |
| 41 | 1 | R101 | RES SMD 2.2Ω 5% 1/3W 1206 | Stackpole Electronics Inc. | RPC1206JT2R20 |
| 42 | 1 | T1 | Flyback Transformer 3.2mH | Kunshan Eagerness Electronics Co., Ltd | PQ20401-802 A |
| 43 | 1 | U1 | IC REG CTRLR FLYBK ISO 7SOIC | Texas Instruments | UCC28740D |
| 44 | 1 | U9 | IC VREF SHUNT ADJ SOT23-3 | Nexperia USA Inc. | TL431AQDBZR,215 |
| 45 | 1 | U11 | OPTOISOLATR 5kV TRANSISTOR 4-SOP | Vishay Semiconductor Opto Division | TCLT1003 |
| | - | | | , contraction opto bitision | |

Wolfspeed. A CREE COMPANY Downloaded from Arrow.com.

© 2018 Cree, Inc. All rights reserved